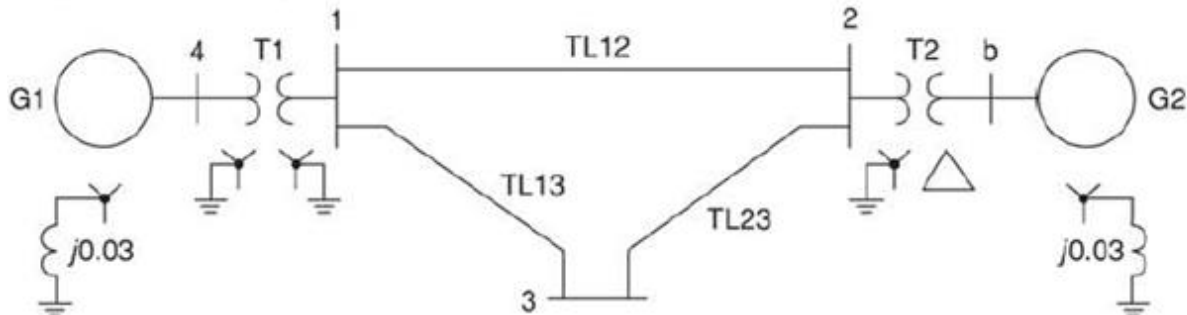


Çankaya University  
Electrical & Electronics Engineering Department  
EE 465 Power Systems Homework # 4

1-

Equipment ratings and per-unit reactances for the system shown in Figure are given as follows:



Synchronous generators:

G1    100 MVA    25 kV     $X_1 = X_2 = 0.2$      $X_0 = 0.05$

G2    100 MVA    13.8 kV     $X_1 = X_2 = 0.2$      $X_0 = 0.05$

Transformers:

T1    100 MVA    25/230 kV     $X_1 = X_2 = X_0 = 0.05$

T2    100 MVA    13.8/230 kV     $X_1 = X_2 = X_0 = 0.05$

Transmission lines:

TL12    100 MVA    230 kV     $X_1 = X_2 = 0.1$      $X_0 = 0.3$

TL13    100 MVA    230 kV     $X_1 = X_2 = 0.1$      $X_0 = 0.3$

TL23    100 MVA    230 kV     $X_1 = X_2 = 0.1$      $X_0 = 0.3$

Using a 100-MVA, 230-kV base for the transmission lines, draw the per-unit sequence networks and reduce them to their Thévenin equivalents, “looking in” at bus 3. Neglect  $\Delta$ -Y phase shifts. Compute the fault currents for a bolted three-phase fault at bus 3.


2-

A 500-MVA, 13.8-kV synchronous generator with  $X_d'' = X_2 = 0.20$  and  $X_0 = 0.05$  per unit is connected to a 500-MVA, 13.8-kV  $\Delta/500$ -kV Y transformer with 0.10 per-unit leakage reactance. The generator and transformer neutrals are solidly grounded. The generator is operated at no-load and rated voltage, and the high-voltage side of the transformer is disconnected from the power system. Compare the subtransient fault currents for the following bolted faults at the transformer high-voltage terminals: three-phase fault, single line-to-ground fault, line-to-line fault, and double line-to-ground fault.


**Çankaya University**  
**Electrical & Electronics Engineering Department**  
**EE 465 Power Systems Homework # 4**

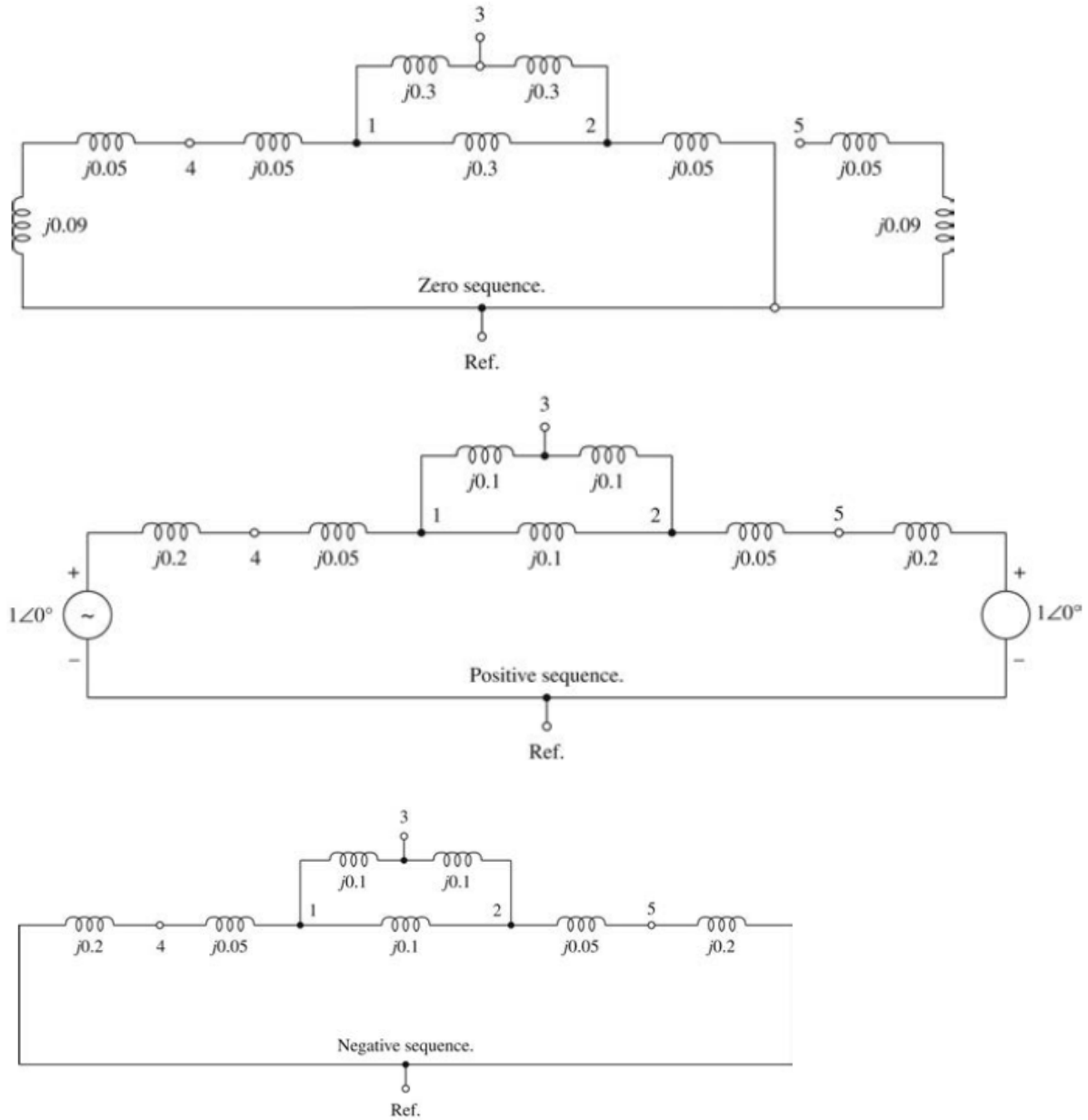**HW41 SOL**


The zero-, positive-, and negative sequence networks are shown below:



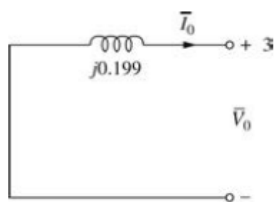
Using delta-wye transformation and series-parallel combinations, thevenin equivalents looking into bus 3 are shown below:



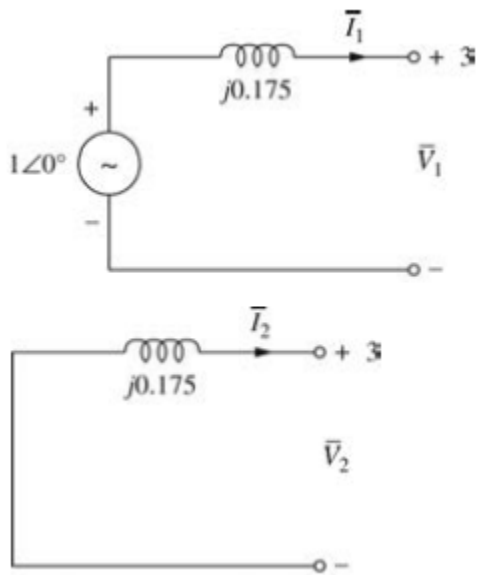Çankaya University  
Electrical & Electronics Engineering Department  
EE 465 Power Systems Homework # 4



For a bolted 3-phase fault at bus 3,

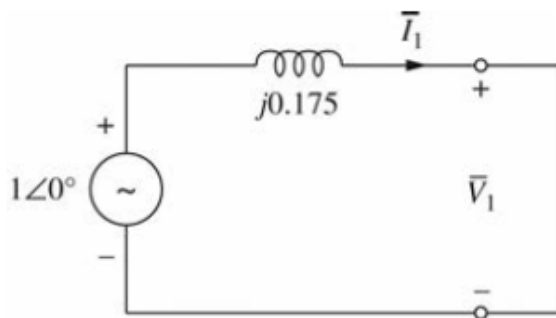

$$\bar{V}_1 = 0; \text{ Also } \bar{V}_2 = \bar{V}_0 = 0$$


$$\bar{I}_0 = 0; \bar{I}_2 = 0$$

$$\bar{I}_1 = \frac{1\angle 0^\circ}{j0.175} = -j5.71$$

The fault current is 5.71 pu.

$$\begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 \\ -j5.71 \\ 0 \end{bmatrix} = \begin{bmatrix} 5.71\angle -90^\circ \\ 5.71\angle 150^\circ \\ 5.71\angle 30^\circ \end{bmatrix}$$

HW42 SOL

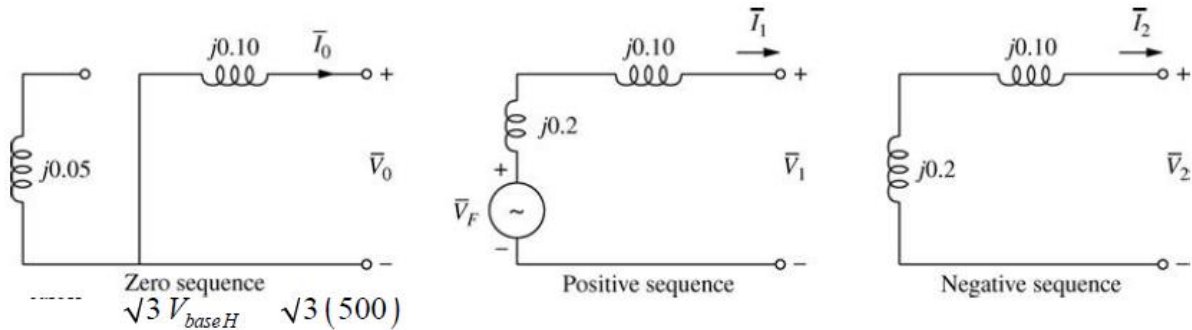

**Three-phase fault:**

$$\bar{I}_0 = \bar{I}_2 = 0 \quad \bar{I}_1 = \frac{\bar{V}_F}{\bar{Z}_1} = \frac{1.0 \angle 0^\circ}{j0.30} = -j3.333 \text{ per unit}$$

$$\bar{I}_a'' = \bar{I}_1 = -j3.333 \text{ per unit} = \underline{\underline{-j1.925 \text{ kA}}}$$

**Single line-to-ground fault:**

$$\bar{I}_0 = \bar{I}_1 = \bar{I}_2 = \frac{\bar{V}_F}{\bar{Z}_0 + \bar{Z}_1 + \bar{Z}_2} = \frac{1.0 \angle 0^\circ}{j(0.1 + 0.3 + 0.3)} = -j1.429 \text{ per unit}$$

$$\bar{I}_a'' = 3\bar{I}_0 = -j4.286 \text{ per unit} = \underline{\underline{-j2.474 \text{ kA}}}$$

**Line-to-line fault:**

$$\bar{I}_0 = 0 \quad \bar{I}_1 = -\bar{I}_2 = \frac{\bar{V}_F}{\bar{Z}_1 + \bar{Z}_2} = \frac{1.0 \angle 0^\circ}{j(0.3 + 0.3)} = -j1.667 \text{ per unit}$$

$$\bar{I}_b'' = (a^2 - a)\bar{I}_1 = (a^2 - a)(-j1.667) = 2.887 \angle 180^\circ \text{ per unit}$$

$$\bar{I}_b'' = \underline{\underline{1.667 \angle 180^\circ \text{ kA}}}$$

Çankaya University  
Electrical & Electronics Engineering Department  
EE 465 Power Systems Homework # 4

**Double line-to-ground fault:**

$$\bar{I}_1 = \frac{\bar{V}_F}{\bar{Z}_1 + \bar{Z}_2 \parallel \bar{Z}_0} = \frac{1.0 \angle 0^\circ}{j(0.3 + 0.3 \parallel 0.1)} = \frac{1.0}{j0.375} = -j2.667 \text{ per unit}$$

$$\bar{I}_2 = -\bar{I}_1 \left( \frac{\bar{Z}_0}{\bar{Z}_0 + \bar{Z}_2} \right) = (j2.667) \left( \frac{.1}{.4} \right) = j0.667 \text{ per unit}$$

$$\bar{I}_0 = -\bar{I}_1 \left( \frac{\bar{Z}_2}{\bar{Z}_0 + \bar{Z}_2} \right) = (j2.667) \left( \frac{.3}{.4} \right) = j2.0 \text{ per unit}$$

$$\begin{aligned} \bar{I}_B'' &= \bar{I}_c + a^2 \bar{I}_1 + a \bar{I}_2 = 2.0 \angle 90^\circ + 2.667 \angle 150^\circ + .667 \angle 210^\circ = 4.163 \angle 134^\circ \text{ per unit} \\ &= \underline{\underline{2.404 \angle 134^\circ \text{ kA}}} \end{aligned}$$